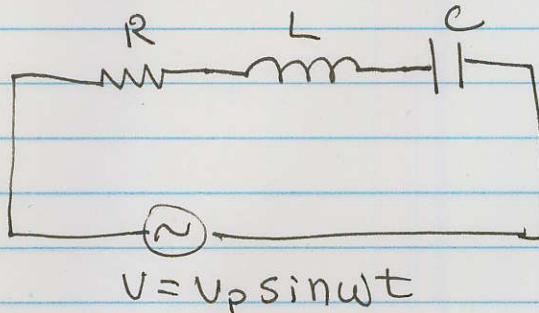


The RLC Series Circuit



Objective 1. To determine the phase angle " ϕ " between the current and applied voltage.

2. Determine " I_p " where
 $I = I_p \sin(\omega t + \phi)$

- First, note that since the elements are in series, the current everywhere in the circuit must be the same at any instant.
- That is, the ac current at all points in a series ac circuit has the same amplitude and phase.

As we found out earlier, the voltage across each element will have different amplitudes and phases.

ELI
ICE

$$V_R = I_p R \sin \omega t = V_{Rp} \sin \omega t$$

$$V_L = I_p X_L \sin\left(\omega t + \frac{\pi}{2}\right) = V_{Lp} \cos \omega t$$

$$V_C = I_p X_C \sin\left(\omega t - \frac{\pi}{2}\right) = -V_{Cp} \cos \omega t$$

X_C = capacitive reactance

X_L = inductive reactance

Where V_{RP} , V_{LP} , and V_{CP} are the peak voltages across each element.



$$V_{RP} = I_p R$$

$$X_L = \omega L$$

$$V_{LP} = I_p X_L$$

$$X_C = \frac{1}{\omega C}$$

$$V_{CP} = I_p X_C$$

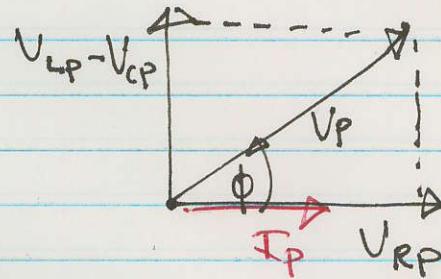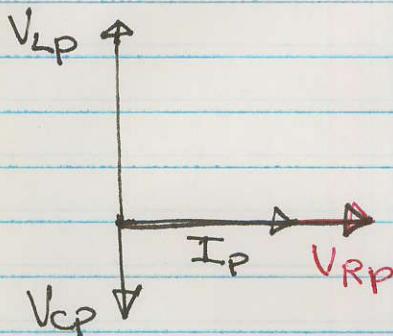

$$V_p = \sqrt{V_{RP}^2 + (V_{LP} - V_{CP})^2}$$

$$V_p = \sqrt{(I_p R)^2 + (I_p X_L - I_p X_C)^2}$$

$$\boxed{V_p = I_p \sqrt{R^2 + (X_L - X_C)^2}}$$

$$X_L = \omega L$$

$$X_C = \frac{1}{\omega C}$$

$$I_p = \frac{V_p}{\sqrt{R^2 + (X_L - X_C)^2}}$$

We define the impedance of the circuit by the following expression:

$$Z = \sqrt{R^2 + (X_L - X_C)^2} \quad (\text{Impedance})$$

$$V_P = I_P Z$$

From the phasor diagram:

$$\tan \phi = \frac{V_{LP} - V_{CP}}{V_{RP}} = \frac{I_P X_L - I_P X_C}{I_P R}$$

$$\tan \phi = \frac{X_L - X_C}{R}$$

$$\phi = \tan^{-1} \left(\frac{X_L - X_C}{R} \right)$$

" ϕ " is the phase angle between the current and voltage.

For example:

When $X_L > X_C$ then $\phi > 0$
 \Rightarrow the current lags behind the applied voltage

When $X_L < X_C$ then $\phi < 0$
 \Rightarrow the current leads the applied voltage

↑ circuit + is
pure resistive

When $X_L = X_C$ then $\phi = 0$

\Rightarrow current and applied voltage are in phase

$$I_p = \frac{V_p}{\sqrt{R^2 + (X_L - X_C)^2}} = \frac{V_p}{R}$$

The frequency at which this occurs is called the resonance frequency.

$$X_L = X_C$$

$$\omega_0 L = \frac{1}{\omega_0 C}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

Resonance Frequency

Graph of I_p :

$$I_p = \frac{V_p}{Z} = \frac{V_p}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}}$$

